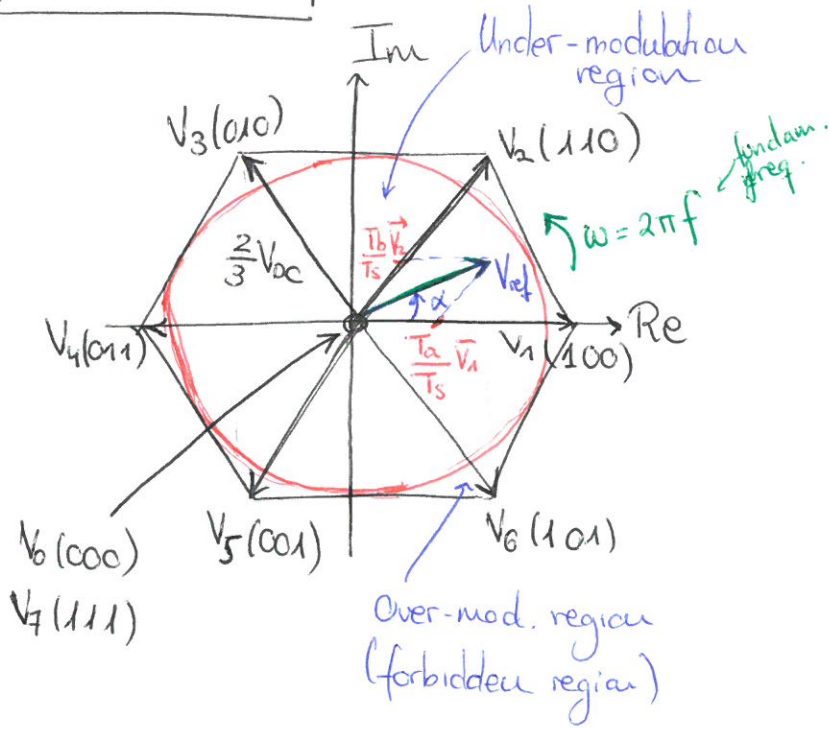


# SVPWM

"Matlab/Simulink Implementation..."

①




\* Space vector:

$$(1) \vec{V}(t) = \frac{2}{3} [V_a(t)e^{j0} + V_b(t)e^{j\frac{2\pi}{3}} + V_c(t)e^{-j\frac{2\pi}{3}}]$$

It maintains its magnitude at any given time. As time increases the angle of the space vector ( $\alpha$ ) increases, causing the vector to rotate with frequency equal to fundamental freq.

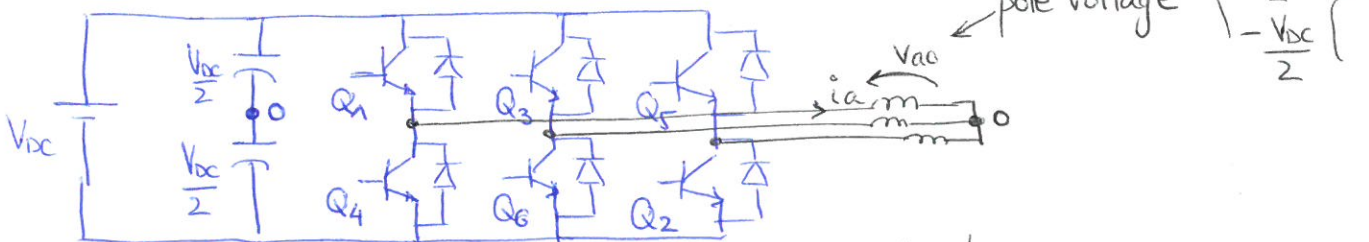\* VSI  $\rightarrow$  8 switching states  $\left\{ \begin{array}{l} \text{Six active states (1-6)} \\ \text{Two zero states (0 and 7)} \end{array} \right.$   
 $\hookrightarrow$  Represented as binary codes.



Example:  $Q_1, Q_6$  and  $Q_2$  closed  $\rightarrow \left\{ \begin{array}{l} V_{ao} = V_{dc}/2 \\ V_{bo} = -V_{dc}/2 \\ V_{co} = -V_{dc}/2 \end{array} \right.$

State denoted as 100 and according to (1)  $\rightarrow \vec{V}(t) = \frac{2}{3} \cdot [V_{dc}e^{j0}]$

In each switching state the vector identification uses a '0' to represent the negative phase voltage and a '1' the positive.

$$\vec{V}_k = \left\{ \begin{array}{ll} \frac{2}{3} V_{dc} \cdot e^{j(k-1)\frac{\pi}{3}} & \text{if } k=1, 2, 3, 4, 5, 6 \\ 0 & \text{if } k=0, 7 \end{array} \right.$$

Space vector	Sw. state	On-state sw.	Vector definition
$\vec{V}_0$	000	$S_4, S_6, S_2$	$\vec{V}_0 = 0$
$\vec{V}_1$	100	$S_1, S_6, S_2$	$\vec{V}_1 = \frac{2}{3} V_{dc} e^{j0}$
$\vec{V}_2$	110	$S_1, S_3, S_2$	$\vec{V}_2 = \frac{2}{3} V_{dc} e^{j\pi/3}$
$\vec{V}_3$	010	$S_4, S_3, S_2$	$\vec{V}_3 = \frac{2}{3} V_{dc} e^{j2\pi/3}$
$\vec{V}_4$	011	$S_4, S_3, S_5$	$\vec{V}_4 = \frac{2}{3} V_{dc} e^{j\pi}$
$\vec{V}_5$	001	$S_4, S_6, S_5$	$\vec{V}_5 = \frac{2}{3} V_{dc} e^{j4\pi/3}$
$\vec{V}_6$	101	$S_1, S_6, S_5$	$\vec{V}_6 = \frac{2}{3} V_{dc} e^{j5\pi/3}$
$\vec{V}_7$	111	$S_1, S_3, S_5$	$\vec{V}_7 = \frac{2}{3} V_{dc} \cdot e^{j2\pi}$

- 1) Calculate angle  $\theta$  and  $|\vec{V}_{ref}|$  based on input voltage components.
- 2) Calculate modulation index and determine if it's in overmodulation region.
- 3) Find sector in which  $\vec{V}_{ref}$  lies, and the adjacent space vectors  $\vec{V}_k$  and  $\vec{V}_{k+1}$  based on sector angle  $\theta$ .
- 4) Find  $T_a$ ,  $T_b$  and  $T_c$  based on  $T_s$  and  $\theta$ .
- 5) Determine modulation times for the different switching states.

**1** In SVPWM, the 3-ph output voltage vector is represented by a reference vector that rotates at an angular velocity of  $\omega = 2\pi f$ .

$$\left\{ \begin{array}{l} V_a(t) = V_{ref} \cos(\omega t) \\ V_b(t) = V_{ref} \cos(\omega t - 2\pi/3) \\ V_c(t) = V_{ref} \cos(\omega t + 2\pi/3) \\ V_a(t) + V_b(t) + V_c(t) = 0 \end{array} \right. \quad \left\{ \begin{array}{l} \text{The 3-ph voltages can be represented} \\ \text{in a two-dimensional } \alpha\beta \text{ ref-frame.} \\ \text{The magnitude of each active vector} \\ \text{is } \frac{2}{3} V_{DC} \text{ and they are } 60^\circ \text{ apart.} \end{array} \right.$$

The magnitude of the reference vector is:  $\vec{V}_{ref} = \frac{2}{3} (V_a + V_b e^{j2\pi/3} + V_c e^{-j2\pi/3})$

$$|\vec{V}_{ref}| = \sqrt{V_\alpha^2 + V_\beta^2} \quad ; \quad \theta = \tan^{-1} \left( \frac{V_\beta}{V_\alpha} \right)$$

**2** Linear region  $\rightarrow \vec{V}_{ref}$  always remains within the hexagon.

Applying Fourier analysis the fundamental voltage amplitude is:

$$V_{max-sixstep} = \frac{4}{\pi} \left[ \int_0^{\pi/3} \frac{V_{DC}}{3} \sin \theta d\theta + \int_{\pi/3}^{\pi/2} \frac{2}{3} V_{DC} \sin \theta d\theta \right] = \frac{2 V_{DC}}{\pi}$$

The ratio between  $\vec{V}_{ref}$  and the fundamental peak value of the square phase voltage wave  $\left( \frac{2V_{DC}}{\pi} \right)$  is called modulation index. This MI indicates the mode of operation  $\rightarrow \boxed{MI = \frac{|\vec{V}_{ref}|}{V_{max-sixstep}}}$

The max. modulation index is obtained when  $\vec{V}_{ref}$  equals the radius of the inscribed circle:

$$MI_{max} = \frac{\frac{2}{3} V_{DC} \cdot \cos(\pi/6)}{\frac{2 V_{DC}}{\pi}} \approx 0.907$$



[3] Necessary to determine the sector in which  $\vec{V}_{ref}$  lies in order to determine switching time and sequence.

Depending on  $V_x$  and  $V_y$ , the angle of the reference vector is used to determine the sector.

Sector	Degrees
1	$0 < \theta \leq 60^\circ$
2	$60^\circ < \theta \leq 120^\circ$
3	$120^\circ < \theta \leq 180^\circ$
4	$180^\circ < \theta \leq 240^\circ$
5	$240^\circ < \theta \leq 300^\circ$
6	$300^\circ < \theta \leq 360^\circ$

[4]  $T_a, T_b$  and  $T_o$

Modulation vector  $\vec{V}_{ref}$  is mapped onto two adjacent vectors:

$$\vec{V}_k = \frac{2}{3} V_{dc} \cdot e^{j(k-1)\frac{\pi}{3}} = \frac{2}{3} V_{dc} \cdot \left[ \cos(k-1)\frac{\pi}{3} + j \sin(k-1)\frac{\pi}{3} \right]$$

$$\vec{V}_{k+1} = \frac{2}{3} V_{dc} \cdot e^{jk\frac{\pi}{3}} = \frac{2}{3} V_{dc} \cdot \left[ \cos \frac{k\pi}{3} + j \sin \frac{k\pi}{3} \right]$$

Due to symmetry in the patterns in the six sectors the integration can be carried out only half of the PWM period ( $\frac{T_s}{2}$ ):

$$\int_0^{T_s/2} \vec{V}_{ref} dt = \int_0^{T_o/4} \vec{V}_0 dt + \int_{T_o/4}^{T_o/4+T_a} \vec{V}_k dt + \int_{T_o/4+T_a}^{T_o/4+T_a+T_b} \vec{V}_{k+1} dt + \int_{T_o/4+T_a+T_b}^{T_s/2} \vec{V}_7 dt$$

$$\int_0^{T_o/4} \vec{V}_0 dt = \int_{T_o/4+T_a+T_b}^{T_s/2} \vec{V}_7 dt = 0 \leftarrow \text{Zero voltages at null states!}$$

$$\left\{ \begin{array}{l} \vec{V}_{ref} \frac{T_s}{2} = \vec{V}_k \cdot T_a + \vec{V}_{k+1} \cdot T_b \\ \vec{V}_{ref} = V_x + j V_y \end{array} \right. \left\{ \begin{array}{l} T_a \text{ and } T_b \text{ denote the required} \\ \text{on-time of } \vec{V}_k \text{ and } \vec{V}_{k+1} \text{ during} \\ \text{each sample period, } k \text{ is the} \\ \text{sector number denoting } \vec{V}_{ref} \text{ location.} \end{array} \right.$$

$$\begin{bmatrix} V_x \\ V_y \end{bmatrix} \frac{T_s}{2} = \frac{2V_{dc}}{3} \left( T_a \begin{bmatrix} \cos \frac{(k-1)\pi}{3} \\ \sin \frac{(k-1)\pi}{3} \end{bmatrix} + T_b \cdot \begin{bmatrix} \cos \frac{k\pi}{3} \\ \sin \frac{k\pi}{3} \end{bmatrix} \right) \rightarrow$$

$$\begin{bmatrix} T_a \\ T_b \end{bmatrix} = \frac{\sqrt{3} T_s}{2 V_{dc}} \begin{bmatrix} \sin k\pi/3 & -\cos k\pi/3 \\ -\sin (k-1)\pi/3 & \cos (k-1)\pi/3 \end{bmatrix} \begin{bmatrix} V_\alpha \\ V_\beta \end{bmatrix}$$

$$\vec{V}_{ref} = |\vec{V}_{ref}| e^{j\omega t} = |\vec{V}_{ref}| (\cos \omega t + j \sin \omega t)$$

$$\begin{bmatrix} T_a \\ T_b \end{bmatrix} = \frac{\sqrt{3} T_s \cdot |\vec{V}_{ref}|}{2 V_{dc}} \begin{bmatrix} \sin k\pi/3 & -\cos k\pi/3 \\ -\sin (k-1)\pi/3 & \cos (k-1)\pi/3 \end{bmatrix} \begin{bmatrix} \cos n\omega T_s \\ \sin n\omega T_s \end{bmatrix}$$


$$MI = \frac{|\vec{V}_{ref}|}{\frac{2 V_{dc}}{\pi}}; |\vec{V}_{ref}| = \frac{MI \cdot 2 V_{dc}}{\pi}$$

$$\begin{bmatrix} T_a \\ T_b \end{bmatrix} = \frac{MI \sqrt{3} T_s}{\pi} \begin{bmatrix} * \\ * \end{bmatrix} \begin{bmatrix} \cos n\omega T_s \\ \sin n\omega T_s \end{bmatrix} \quad (*)$$

Since the sum of  $2T_a$  and  $2T_b$  (due to symmetry) should be less than or equal to  $T_s$ , the inverter has to stay in the zero stage for the rest of the period:


$$T_s = T_0 + 2(T_a + T_b) \rightarrow T_0 = T_s - 2(T_a + T_b)$$

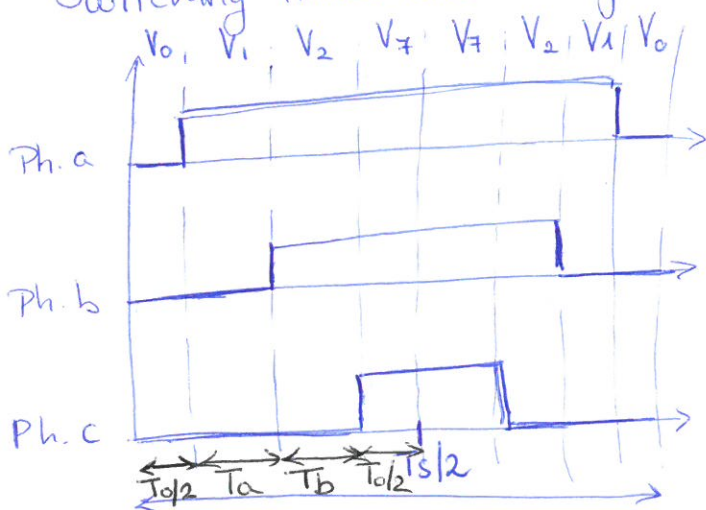Switching times are arranged symmetrical around the center of  $T_s$ .



$\vec{V}_7$  is placed at the center of  $T_s$  and  $\vec{V}_0$  at the start and end and the total period for a zero vector is divided equally among the two zero vectors.

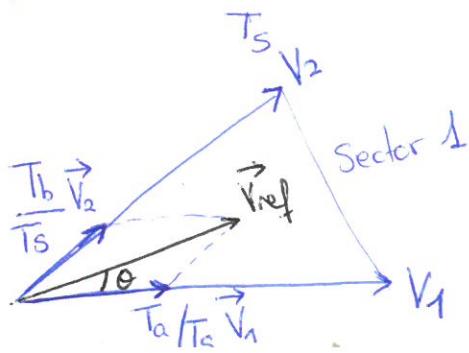The symmetrical PWM signal is preferred because it has the lowest harmonic distortion (THD).



$$(*) \quad T_a = \frac{\sqrt{3} \cdot MI \cdot T_s}{\pi} \sin(k\pi/3 - \underbrace{n\omega T_s}_{\theta})$$

$$T_b = \frac{\sqrt{3} \cdot MI \cdot T_s}{\pi} \sin(\underbrace{n\omega T_s}_{\theta} - \underbrace{(k+1)\pi/3}_{\alpha})$$

### 5 Determination of Switching times for each transistor switch


- Necessary to arrange switching sequence so that  $f_s$  of each inverter leg is minimized
- Two minimum switch losses, only 2 adjacent <sup>active</sup> vectors and two zero vectors are used in a sector. This means that each switching period starts with one zero vector and ends with one zero vector.
- Therefore, the switching cycle of the output voltage is double the sampling time, and the two output voltage waveforms become symmetrical
- In order to reduce the switch. loss it's required that at each time only one bridge arm is switched.

Sector	Switching seq.
1	$V_0 - V_1 - V_2 - V_7 - V_2 - V_1 - V_0$
2	$V_0 - V_3 - V_2 - V_7 - V_2 - V_3 - V_0$
3	$V_0 - V_3 - V_4 - V_7 - V_4 - V_3 - V_0$
4	$V_0 - V_5 - V_4 - V_7 - V_4 - V_5 - V_0$
5	$V_0 - V_5 - V_6 - V_7 - V_6 - V_5 - V_0$
6	$V_0 - V_1 - V_6 - V_7 - V_6 - V_1 - V_0$


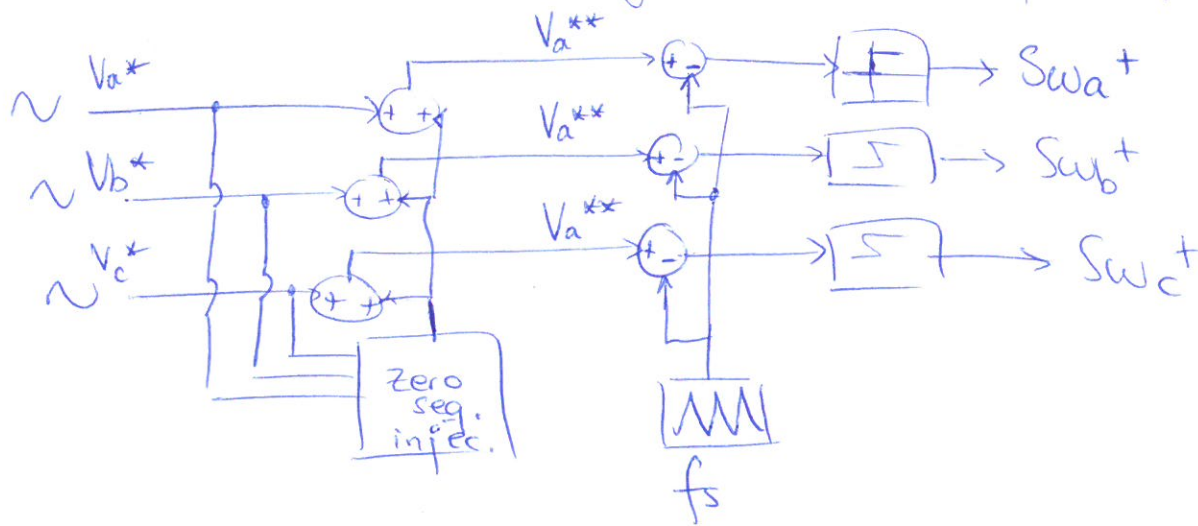
# Modulation

\* Zero sequence injection (chapter 2. pg 32 Rik.) "Simple analytical ... (paper)"



- Improve waveform quality
- Reduce switching losses
- It doesn't affect inverter's L-L voltage but influences switching freq. characteristics.

← fundamental freq.

$$V_a^{**} = V_a^* + V_0 = V_{1m}^* \cos(\omega t) + V_0$$

$$V_b^{**} = V_b^* + V_0 = V_{1m}^* \cos(\omega t - \frac{2\pi}{3}) + V_0$$

$$V_c^{**} = V_c^* + V_0 = V_{1m}^* \cos(\omega t + \frac{2\pi}{3}) + V_0$$

↳ SVPWM → Zero seq. calculation using minimum magnitude test.

Compares magnitudes of  $V_a^*$ ,  $V_b^*$  and  $V_c^*$  and selects signal with minimum magnitude. Scaling this signal by  $\frac{1}{2}$  the zero sequence signal is found.

$$\text{Ex. } |V_a^*| \leq |V_b^*|, |V_c^*| \rightarrow V_0 = \frac{1}{2} \cdot V_a^*$$

\* According to Rik:


$$U_0^* = -\frac{1}{2} \left[ \max \{U_a^*, U_b^*, U_c^*\} + \min \{U_a^*, U_b^*, U_c^*\} \right]$$

- This approach, known as pulse centering unit, SYMMETRIZES the max and min average voltage references with respect to the true axis
- Possible to increase the space vector amplitude from  $|U^*| = \sqrt{\frac{3}{8}} U_{dc}$  to  $|\bar{U}^*| = \sqrt{\frac{1}{2}} U_{dc} \rightarrow \text{increase} \simeq 15\%$

$$U^* = \sqrt{\frac{2}{3}} (U_a^* + U_b^* e^{j120^\circ} + U_c^* e^{j240^\circ}) - \sqrt{\frac{2}{3}} U_0 \cdot \underbrace{(1 + e^{j120^\circ} + e^{j240^\circ})}_0$$

- Pulse centering unit important to maximize the linear operating region of the inverter. ( $\simeq 15\%$ ) allowing the inverter to be operated with higher ~~reference~~ voltages and consequently lower currents.

# || SVPWM ||

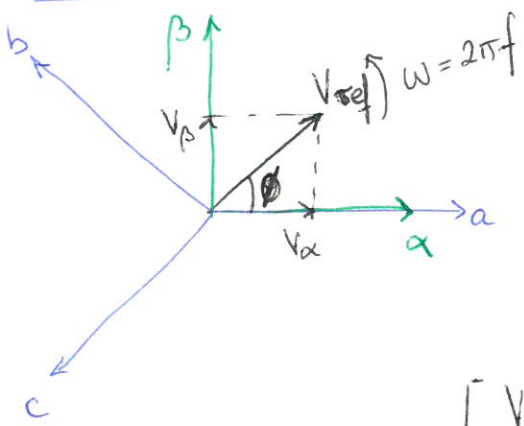

$$\begin{cases} V_{AN} = V_m \cdot \sin(2\pi f t) \\ V_{BN} = V_m \cdot \sin(2\pi f t - 2\pi/3) \\ V_{CN} = V_m \cdot \sin(2\pi f t + 2\pi/3) \end{cases}$$


Controlled according to the rotation of the space vector  $V_{ref}$ .

$$\begin{bmatrix} V_{AN} \\ V_{BN} \\ V_{CN} \end{bmatrix} = \frac{1}{3} \cdot \begin{bmatrix} 2 & -1 & -1 \\ -1 & 2 & -1 \\ -1 & -1 & 2 \end{bmatrix} \begin{bmatrix} V_{AO} \\ V_{BO} \\ V_{CO} \end{bmatrix}$$

$$\begin{bmatrix} V_{\alpha} \\ V_{\beta} \end{bmatrix} = \frac{2}{3} \begin{bmatrix} 1 & -1/2 & -1/2 \\ 0 & \sqrt{3}/2 & -\sqrt{3}/2 \end{bmatrix} \begin{bmatrix} V_{AN} \\ V_{BN} \\ V_{CN} \end{bmatrix}$$

$$|V_{ref}| = \sqrt{V_{\alpha}^2 + V_{\beta}^2} ; \quad \phi = \tan^{-1}\left(\frac{V_{\beta}}{V_{\alpha}}\right)$$

\* Algorithm for sector determination:

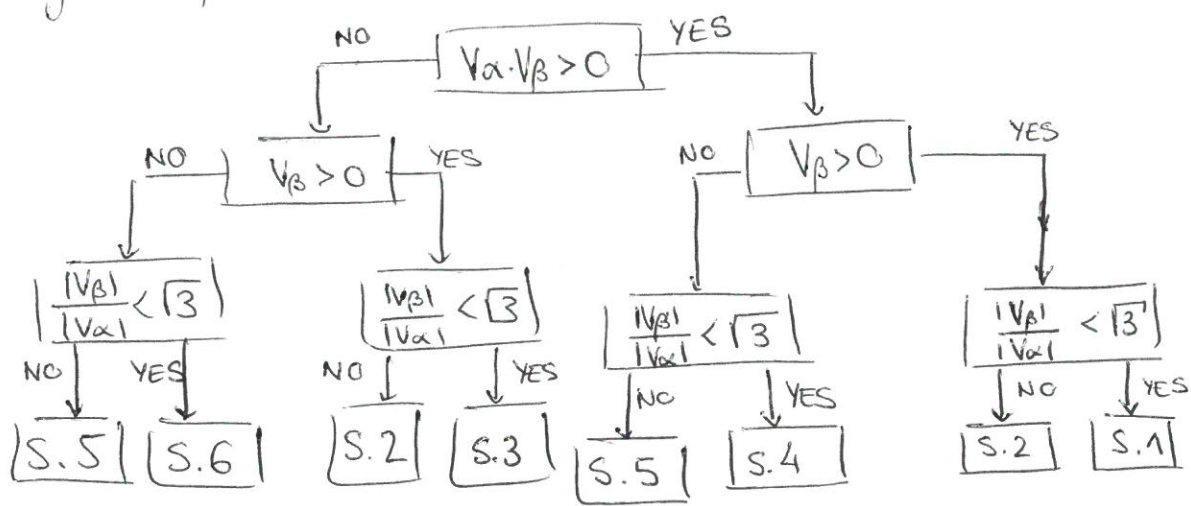

$$* V_{ref} = \frac{T_k}{T_s} \cdot V_k + \frac{T_{k+1}}{T_s} \cdot V_{k+1} \quad , k = 1, 2, \dots, 6 \quad / \quad T_k + T_{k+1} \leq T_s$$

$$V_{ref} \cdot T_s = T_k \cdot V_k + T_{k+1} \cdot V_{k+1} + T_0 V_0 \quad ; \quad T_0 = T_s - T_k - T_{k+1}$$

$$\left\{ \begin{array}{l} \theta = \phi - \frac{k-1}{3}\pi \\ V_{ref} \cdot \sin\left(\frac{\pi}{3} - \theta\right) = \frac{T_k}{T_s} \cdot V_k \cdot \sin(\pi/3) \\ V_{ref} \cdot \sin(\theta) = \frac{T_{k+1}}{T_s} \cdot V_{k+1} \cdot \sin(\pi/3) \end{array} \right\} \rightarrow \left\{ \begin{array}{l} T_k = \frac{\sqrt{3} \cdot T_s \cdot V_{ref} \cdot \sin\left(\frac{k\pi}{3} - \phi\right)}{V_{DC}} \\ T_{k+1} = \frac{\sqrt{3} \cdot T_s \cdot V_{ref} \cdot \sin\left(\phi - \frac{k-1}{3}\pi\right)}{V_{DC}} \end{array} \right.$$